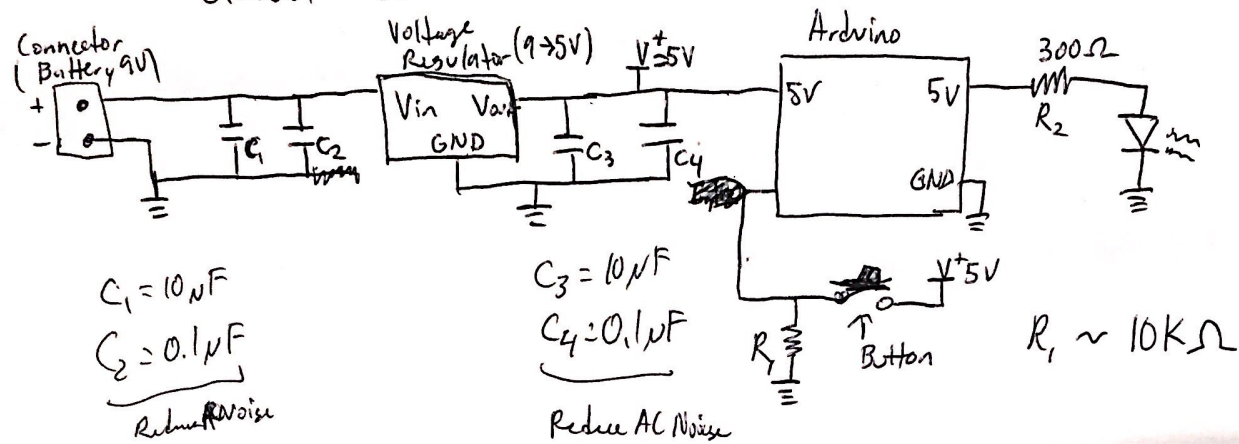


# Circuit Schematic

Eddie Yao



1.4V-2.6V  
 Forward current  $\sim 10mA$